

## BLG 231E - Digital Circuits Assignment 3 Solution Key

**1.a**) fc,d01 00 11 10 00 a,bΦ 01 0 11 Φ 10 0 Φ

The set of all prime implicants: bc'd, a'd, a'b, a'c', b'd', cd'

<b>1.b</b> )				Group B1	0,1	000-	$\rightarrow$
		_		(A1, A2)	0,2	00-0	$\rightarrow$
Group A1	0	0000	<b>→</b>		0,4	0-00	$\rightarrow$
Group A2	1	0001	$\rightarrow$				
	-	<u> </u>			0,8	-000	$\rightarrow$
	2	0010	<b>→</b>	Group B2	1,3	00-1	$\rightarrow$
	4	0100	→ 	(A2, A3)	1,5	0-01	<u> </u>
	8	1000	<i>→</i>		2,3	001-	<b>→</b>
Group A3	3	0011	<b>→</b>		2,6	0-10	<b>—</b> →
	5	0101	<b>→</b>		2,10	-010	<b>—</b>
	6	0110	$\rightarrow$		4,5	010-	$\rightarrow$
	10	1010	<b>—</b>		4,6	01-0	$\rightarrow$
					8,10	10-0	$\rightarrow$
Group A4	13	1101	<i>→</i>	Group B3	6,14	-110	<b>—</b>
	14	1110	<b>→</b>	(A3, A4)	5,13	-101	
				(A3, A4)	3,13	-101	
					10,14	1-10	$\rightarrow$

Group C1	0,1,2,3	00	✓
(B1, B2)	0,1,4,5	0-0-	✓
	0,2,4,6	00	✓
	0,2,8,10	-0-0	✓
Group C2	2,610,14	10	✓
(B1, B2)			•
וטו. טבו			

The set of all prime implicants: bc'd, a'd', a'b', a'c', b'd', cd'

**2.** Prime implicant chart:

	0	1	2	3	4	6	13	a,b,c,d	cost
bc'd							Х	-101	7
a'b'	Х	Х	х	х				00	6
a'c'	Х	Х			х			0-0-	6
a'd'	Х		Х		Х	Х		00	6
b'd'	Х		Х					-0-0	6
cd'			Х			Х		10	5

Selected prime implicants: a'b', bc'd

## Reduced Prime implicant chart:

1								
	4	6	a,b,c,d	cost				
a'c'	Х		0-0-	6				
a'd'	Х	х	00	6				
b'd'			-0-0	6				
cd'		Х	10	5				

Selected prime implicant: a'd'

Minimal expression for the function with the lowest cost:

$$f(a,b,c,d) = a'b' + a'd' + bc'd$$

Total cost: 19