



BLG 231E - Digital Circuits

Assignment 4

Due Date: Thursday, December 1, 2022, 23:59.

- Please prepare your homework using a computer. Points will be taken off for handwritten submissions.
- **Consequences of plagiarism:** Any cheating will be subject to disciplinary action.
- **No late submissions** will be accepted. **Do not send your solutions by e-mail.** We will only accept files uploaded to the official Ninova e-learning system before the deadline. Do not risk leaving your submission to the last few minutes.
- **Submissions:** Submit your solution to Ninova as a **Logisim .circ file** and a **PDF** that briefly explains how your circuit works. Please **write your full name** (first and last name) and Student ID in the box below.

Student ID :


Full Name :

If you have any questions, please e-mail teaching assistant

• Büşranur Bülbül Demir (bulbulb17@itu.edu.tr)

1. The combinational circuit shown on the right performs arithmetic operations on three 4-bit integers, A, B, and C based on the values of inputs x and y, as explained in the table below. We ignore carry, borrow, and overflow for this circuit.

xy	Operation
00	$Z = A + B$
01	$Z = 2A$
10	$Z = B - C$
11	$Z = A - C$

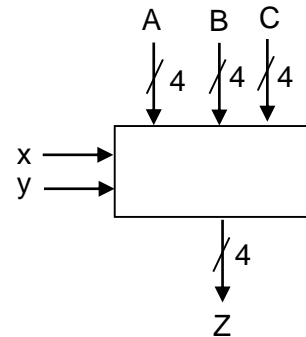

Design this circuit using **only a single parallel adder**, **two 4-bit 2:1 MUXs**, and **NOT gates**. Use **the fewest possible number** of gates and multiplexers to make your circuit design as simple as possible. (**Note:** A 4-bit 2:1 MUX has **two inputs**, each having a **size of 4 bits**.)

Implement and test the circuit using the Logisim tool. Do not show the internal structure of the parallel adder; show it only as a block. Fully label all inputs and outputs. Write your name and student ID at the top of the .circ file.

Explain briefly how your circuit works. Create a pdf file for your explanations.