



BLG 231E - Digital Circuits Assignment 5

Due Date: Thursday, December 22, 2022, 23:59.

- Please **write and draw neatly**.
- Please prepare your homework using a computer. Points will be taken off for handwritten submissions.
- **Consequences of plagiarism:** Any cheating will be subject to disciplinary action.
- **No late submissions** will be accepted. **Do not send your solutions by e-mail.** We will only accept files uploaded to the official Ninova e-learning system before the deadline. Do not risk leaving your submission to the last few minutes.
- **Submissions:** Submit your solution PDF to Ninova. Please **write your full name** (first and last name) and Student ID in the box below.

Student ID :

Full Name :

If you have any questions, please e-mail teaching assistant

- Esin Ece Aydın (aydinesi16@itu.edu.tr)

Analyze the synchronous sequential circuit with a single input (X) and two outputs (A, B) shown in the figure below. **(Note:** One flip-flop is a J-K flip-flop, the other is a D flip-flop).

- Write the next state equations, $S^+ = H(S, I)$.
- Construct the state/output table.
- Draw the state diagram.

