



## BLG 231E - Digital Circuits


### Assignment 4

Student ID: 150200054

Full Name: Ash Yel

1. The combinational circuit shown on the right performs arithmetic operations on three 4-bit integers, A, B, and C based on the values of inputs x and y, as explained in the table below. We ignore carry, borrow, and overflow for this circuit.


xy	Operation
00	$Z = A + B$
01	$Z = 2A$
10	$Z = B - C$
11	$Z = A - C$

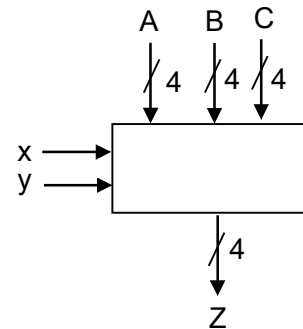

Design this circuit using **only a single parallel adder**, **two 4-bit 2:1 MUXs**, and **NOT gates**. Use **the fewest possible number** of gates and multiplexers to make your circuit design as simple as possible. (**Note:** A 4-bit 2:1 MUX has **two inputs**, each having a **size of 4 bits**.)

Implement and test the circuit using the Logisim tool. Do not show the internal structure of the parallel adder; show it only as a block. Fully label all inputs and outputs. Write your name and student ID at the top of the **.circ** file.

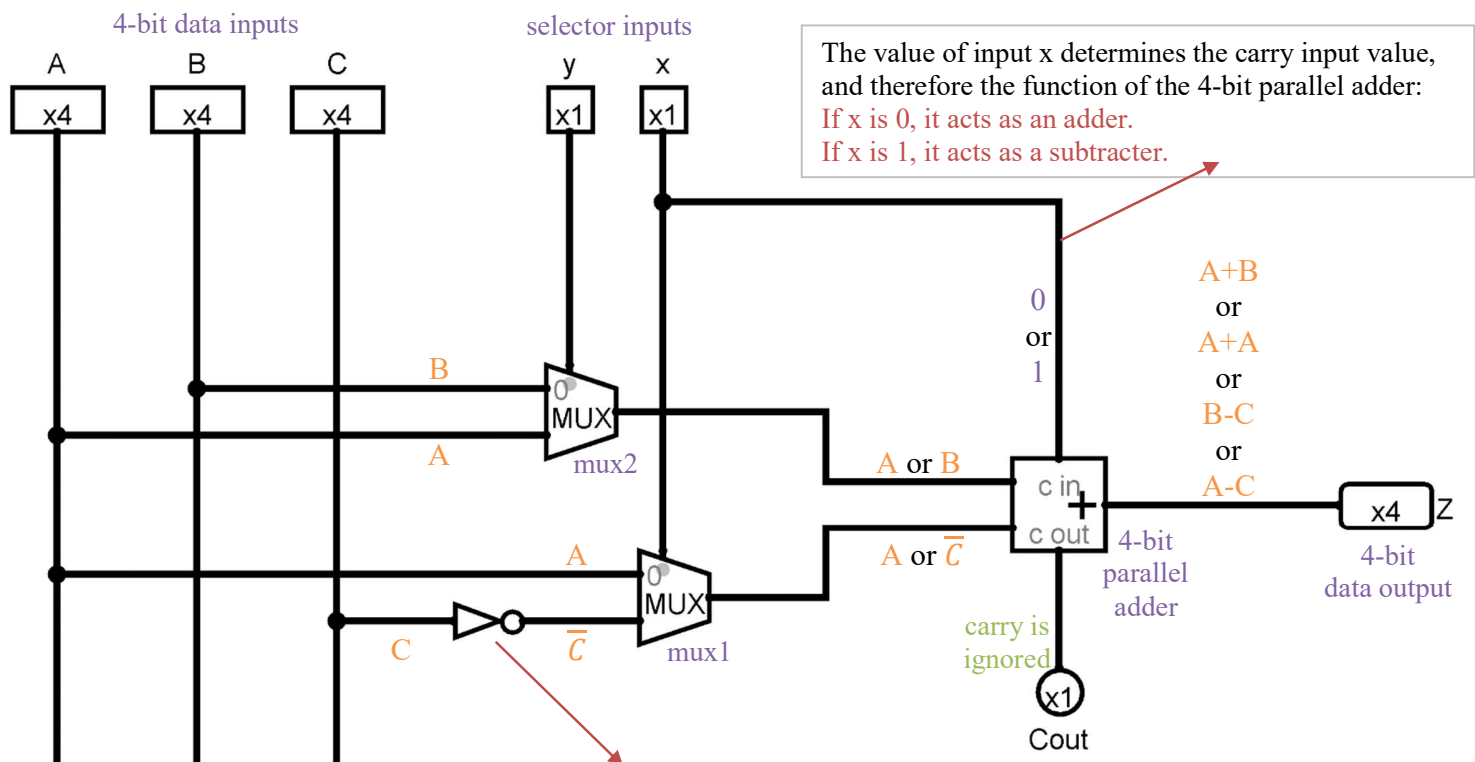Explain briefly how your circuit works. Create a pdf file for your explanations.



x	y	integer selected by mux1	integer selected by mux2	inputs of parallel adder	carry input	What happens through the circuit?	Z
0	0	A	B	A and B	0	$x=0 \rightarrow \text{mux1 selects A}$ $y=0 \rightarrow \text{mux2 selects B}$ $x=0 \rightarrow \text{carry input is 0}$	these are added by the parallel adder $A+B+0 = A+B$
0	1	A	A	A and A	0	$x=0 \rightarrow \text{mux1 selects A}$ $y=1 \rightarrow \text{mux2 selects A}$ $x=0 \rightarrow \text{carry input is 0}$	these are added by the parallel adder $A+A+0 = 2A$
1	0	$\bar{C}$	B	B and $\bar{C}$	1	$x=1 \rightarrow \text{mux1 selects } \bar{C}$ $y=0 \rightarrow \text{mux2 selects B}$ $x=1 \rightarrow \text{carry input is 1}$	these are added by the parallel adder $B+\bar{C}+1 = B-C$
1	1	$\bar{C}$	A	A and $\bar{C}$	1	$x=1 \rightarrow \text{mux1 selects } \bar{C}$ $y=1 \rightarrow \text{mux2 selects A}$ $x=1 \rightarrow \text{carry input is 1}$	these are added by the parallel adder $A+\bar{C}+1 = A-C$